

2. Having the Boolean function $F(X, Y, Z) = XY + YZ + X\bar{Y}$

- Using truth table to get F [2 marks]
- Get the simplified F as SoP (using k-map) [0.75 mark]
- Get the simplified F as PoS (using another k-map) [0.75 mark]
- Is it better to build the function as SoP or PoS and why? [0.5 mark]

	X	Y	Z	\bar{Y}	XY	YZ	$X\bar{Y}$	F
0	0	0	0	1	0	0	0	0
1	0	0	1	1	0	0	0	0
2	0	1	0	0	0	0	0	0
3	0	1	1	0	0	1	0	1
4	1	0	0	1	0	0	1	1
5	1	0	1	1	0	0	1	1
6	1	1	0	0	1	0	0	1
7	1	1	1	0	1	1	0	1
	(0.5 mark)			Each column (0.25 mark) So all (1 mark)				(0.5 mark)

	YZ			
X	00	01	11	10
0			1	
1	1	1	1	1

$$F(X, Y, Z) = X + YZ \quad (0.75 \text{ mark})$$

	YZ			
X	00	01	11	10
0	0	0		0
1				

$$F(X, Y, Z) = (X + Y)(X + Z) \quad (0.75 \text{ mark})$$

For the k-map if all/some the correct terms are mentioned + added unneeded terms, so each added unneeded term gets -0.25 mark (min grade of this part of the question = zero)

It is better to build the function as SoP as it needs one AND and one OR, while building the function using PoS needs two ORs and one AND. (0.5 mark).

3. For the following Boolean Function

$$F(A, B, C, D) = ABC + \bar{A}CD + A\bar{B}CD + AB\bar{C}D + d(0, 8, 9)$$

- List the minterms of the function (show your work). [1 mark]

Q. 3


$$F(A, B, C, D) = ABC + \bar{A}CD + A\bar{B}CD + AB\bar{C}D$$

List The minterms.

	ABCD	
* ABC	1110	14
0.25	1111	15
* $\bar{A}CD$	0011	3
0.25	0111	7
* $A\bar{B}CD$	1011	11
0.25		
* $AB\bar{C}D$	1101	13
0.25		

$$\Rightarrow F(A, B, C, D) = \sum_m (3, 7, 11, 13, 14, 15)$$

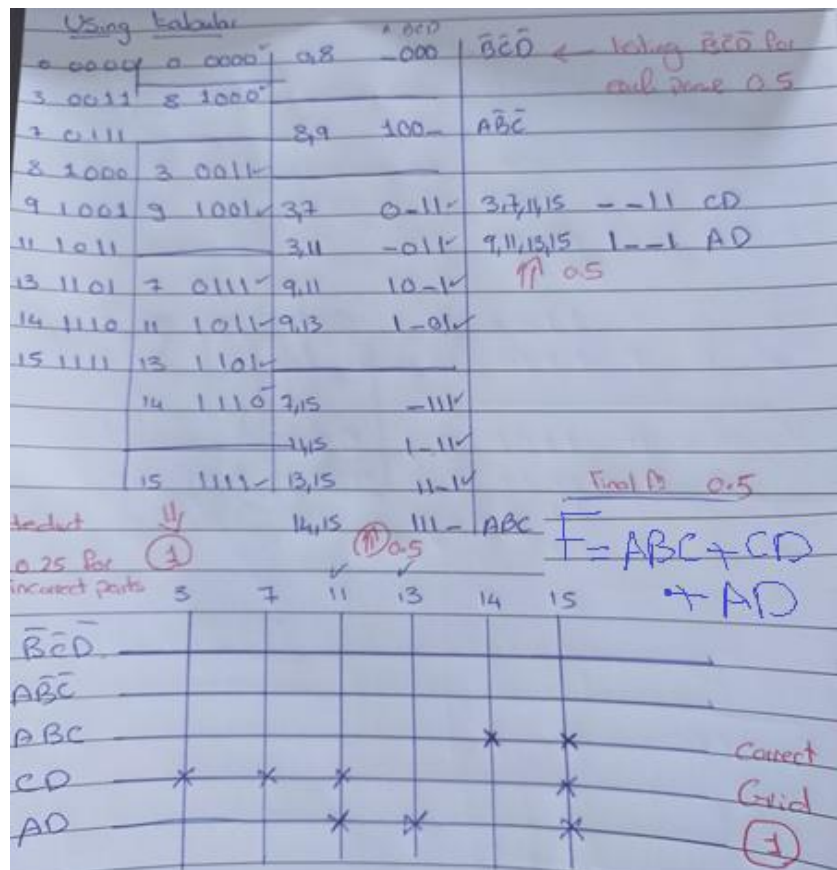- Using tabular method simplify the function (show your work). [4 marks]



4. Design a circuit with 5-input binary input (A,B,C,D,E). It produces a high output F for any prime number detected in the input. Using k-map, get the simplified function as SoP. (No need to put the truth table). Note that a prime number is an integer > 1 that has no positive integer divisors other than 1 and itself. [4 marks]

		A=0			
DE \ BC		00	01	11	10
00				1	1
01			1	1	
11			1		
10				1	

		A=1			
DE \ BC		00	01	11	10
00			1	1	
01				1	
11			1	1	
10					


$$F(A, B, C, D, E) = \bar{B}DE + \bar{A}\bar{B}\bar{C}D + \bar{A}C\bar{D}E + \bar{A}\bar{C}DE + A\bar{B}\bar{C}E + ABCE$$

1 mark to add the 1's on the k-map.

Each term gets 0.5 mark (total =3 marks)


If all/some the correct terms are mentioned + added unneeded terms, so each added unneeded term gets -0.25 mark (min grade of this part of the question =zero)

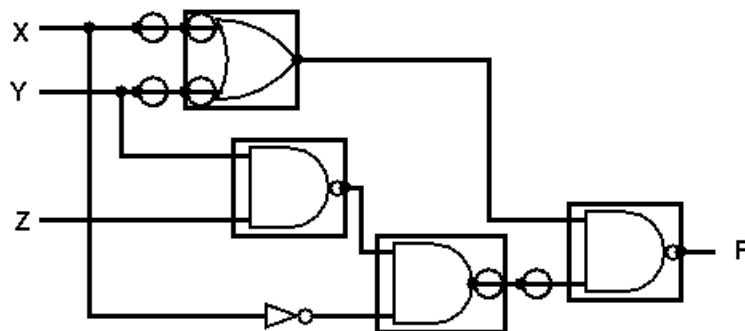5. If the propagation delay of NOT, AND, OR, NANDs are 2, 10, 10, 12 nsec respectively, get the propagation delay [0.5 mark] for the following logic circuit, then build it using only NANDs. [1.5 marks]



Propagation delay of the original circuit = 34 nsec

0.5 mark

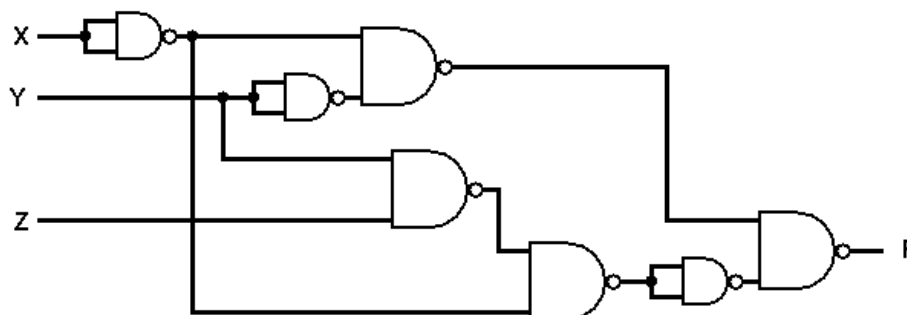

The two already existing NANDs earns 0.25 mark together. Each new NAND earns 0.25 mark (total =1.5 marks).

Each unneeded gate gets -0.25 mark (min grade of this part of the question =zero)