

Quiz 1 (V4)

Name: _____

Id: _____

1. Determine the representation of $(89)_{10}$ using the following code 6421 (1)


any = 10 | 0 10 | 1

2. Add the following two BCD numbers, $(1001\ 0010\ 0011) + (0011\ 0111\ 1000)$ (3)

$$\begin{array}{r}
 \begin{array}{ccc}
 \overset{1}{1} \overset{1}{0} \overset{1}{0} \overset{1}{1} & \overset{1}{0} \overset{1}{0} \overset{1}{1} \overset{1}{0} & \overset{1}{0} \overset{1}{0} \overset{1}{1} \overset{1}{1} \\
 1001 & 0010 & 0011 \\
 + & + & + \\
 \hline
 1100 & 1001 & 1011 \\
 0110 & 0110 & 0110 \\
 + & + & + \\
 \hline
 0001 & 0011 & 0000 & 0001
 \end{array}
 \end{array}$$

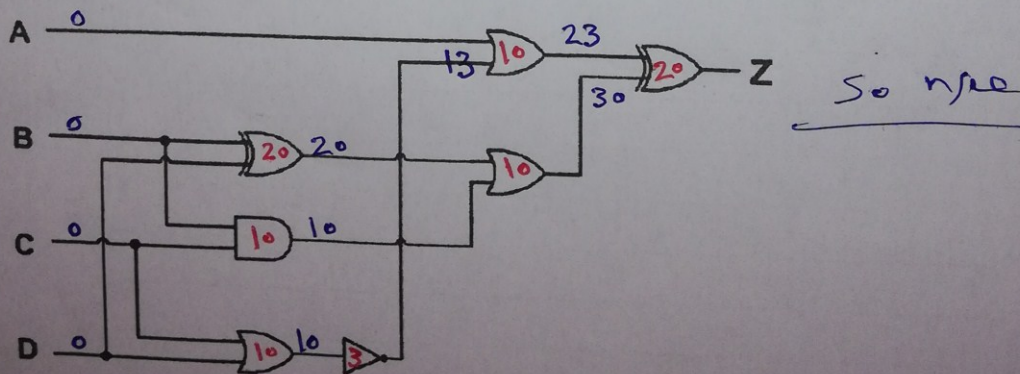3. Calculate the propagation delay of the following logic diagram (1)


Knowing the propagation delay of the following gates: NOT gate=3nsec AND gate & OR gate=10 nsec
 NAND gate & NOR gate=13 nsec XOR gate=20nsec XNOR gate=23 nsec




V4 Cont.

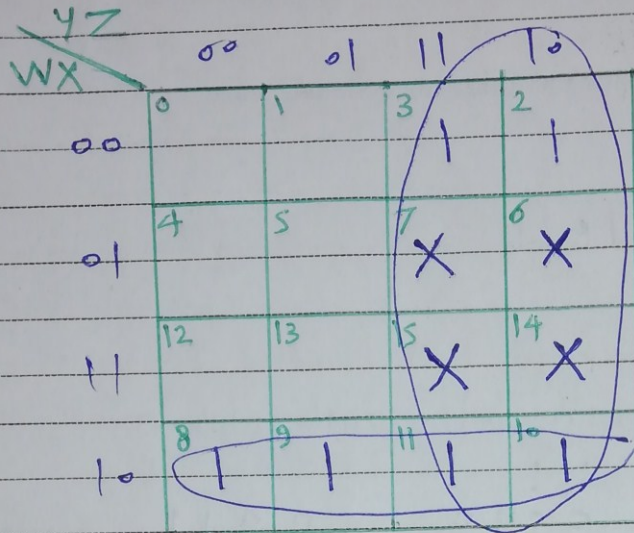4. Draw the logic diagram for the following function after simplification using k-map,
 $F(W,X,Y,Z) = \pi_M(0,1,4,5,12,13) + d(6,7,14,15)$ as SoP (5)

$$F = \sum m(2,3,8,9,10,11) + d(6,7,14,15)$$



$$F_{SOP} = W\bar{X} + Y$$

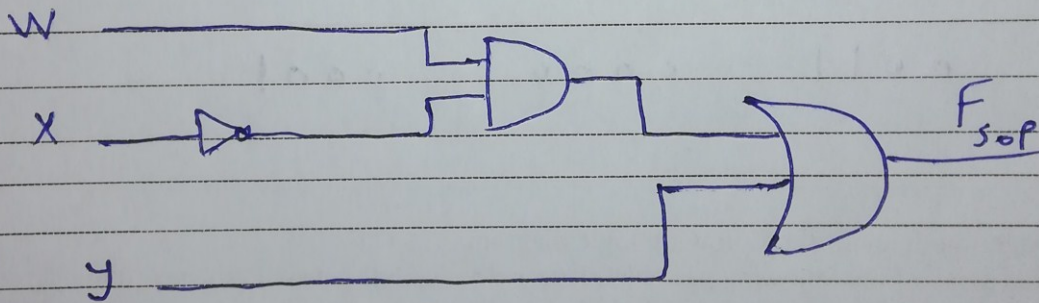

Quiz 1 (V5)

Name: I. Zada Id: _____

1. Determine the representation of $(47)_{10}$ using the following code 5421 (1)

ans = $(0100 \ 1010)$

OR $(0100 \ 0111)$ both answers are correct

2. Add the following two BCD numbers, $(1000 \ 0011 \ 1001) + (0011 \ 0110 \ 0011)$ (3)


$$\begin{array}{r}
 \begin{array}{cccc}
 1 & 0 & 0 & 0 \\
 0 & 0 & 1 & 1
 \end{array}
 +
 \begin{array}{cccc}
 & & 1 & 1 \\
 0 & 0 & 1 & 1 \\
 0 & 1 & 1 & 0
 \end{array}
 +
 \begin{array}{cccc}
 & & 1 & 1 \\
 1 & 0 & 0 & 1 \\
 0 & 0 & 1 & 1
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 \begin{array}{cccc}
 1 & 0 & 1 & 1 \\
 0 & 1 & 1 & 0
 \end{array}
 +
 \begin{array}{cccc}
 1 & 0 & 0 & 1 \\
 0 & 1 & 1 & 0
 \end{array}
 +
 \begin{array}{cccc}
 1 & 1 & 0 & 0 \\
 0 & 1 & 1 & 0
 \end{array}
 \end{array}$$

$$\begin{array}{cccc}
 0 & 0 & 0 & 1 \\
 0 & 0 & 1 & 0 \\
 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0
 \end{array}$$

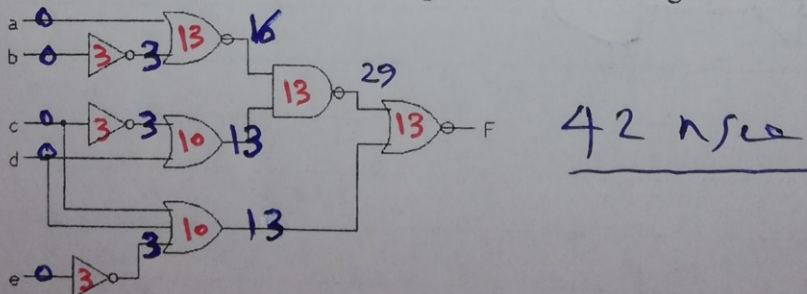3. Calculate the propagation delay of the following logic diagram (1)


Knowing the propagation delay of the following gates: NOT gate=3nsec AND gate & OR gate=10 nsec
 NAND gate & NOR gate=13 nsec XOR gate=20nsec XNOR gate=23 nsec




V5 GAT

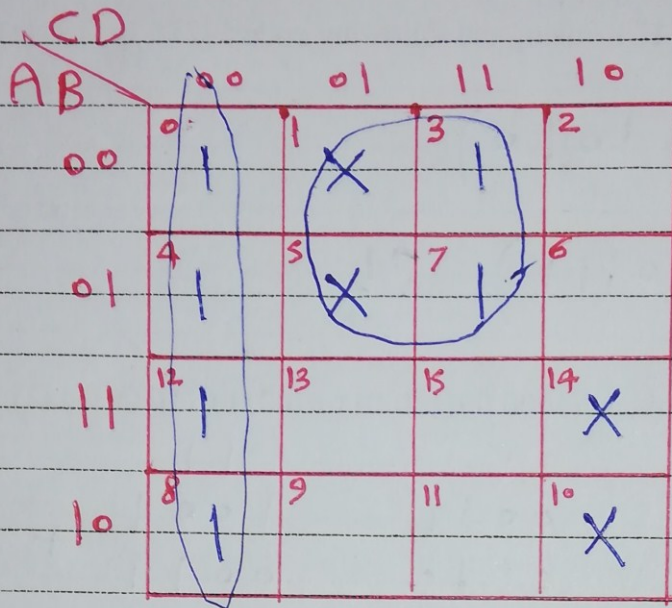4. Draw the logic diagram for the following function after simplification using k-map,
 $F(A,B,C,D) = \pi_M(2,6,9,11,13,15) + d(1,5,10,14)$ as SoP (5)

$$F(A,B,C,D) = \sum m(0,3,4,7,8,12) + d(1,5,10,14)$$



$$F_{SOP} = \bar{C}\bar{D} + \bar{A}D$$

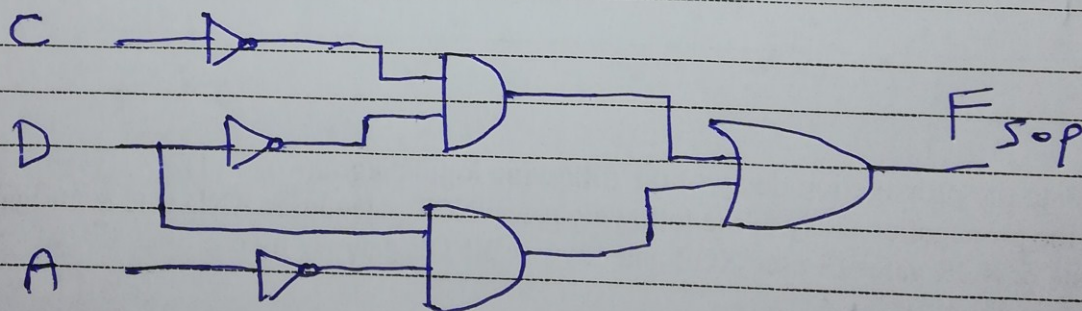

Quiz 1 (V6)

Name: I. Zedan Id: _____


1. Determine the representation of $(93)_{10}$ using the following code 7421 (1)

ans = 1010 0011

2. Add the following two BCD numbers, $(0101\ 1000\ 0110) + (0110\ 0001\ 0110)$ (3)

0101	1000	0110	
0110	0001	0110	+
<hr/>			
1011	1001	1100	
0110	0110	0110	+
<hr/>			
0001	0010	0000	
0010	0000	0010	

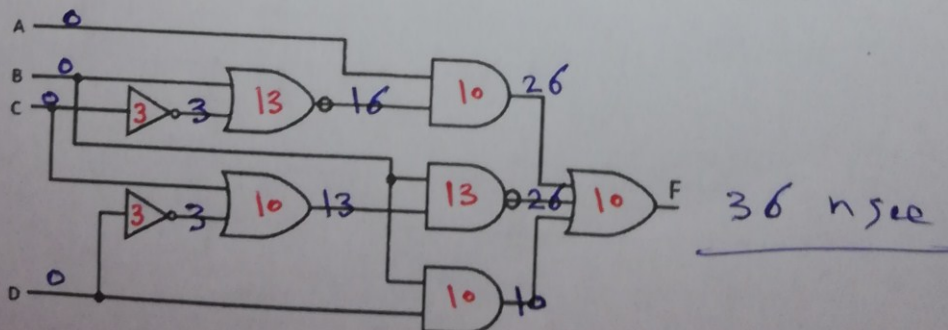
3. Calculate the propagation delay of the following logic diagram (1)
 Knowing the propagation delay of the following gates: NOT gate=3nsec AND gate & OR gate=10 nsec
 NAND gate & NOR gate=13 nsec XOR gate=20nsec XNOR gate=23 nsec



V6 Cont.

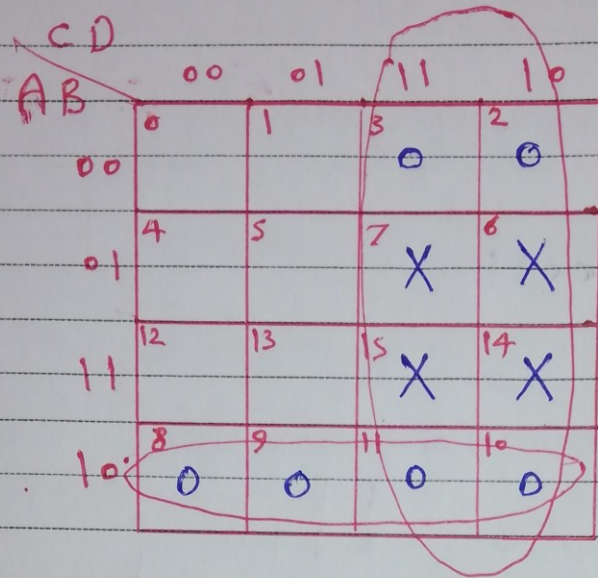4. Draw the logic diagram for the following function after simplification using k-map,
 $F(A,B,C,D) = \sum m(0,1,4,5,12,13) + d(6,7,14,15)$ as PoS (5)

$$F = \prod M(2,3,8,9,10,11) + d(6,7,14,15)$$



$$F_{PoS} = (\bar{A} + B) \cdot \bar{C}$$

