



Faculty of Computers and Artificial Intelligence
Cairo University

Midterm Exam



Program: Computer Science / Software Engineering
Course Name: Computer Organization and Architecture
Course Code: CS331
Instructor(s): Dr. Amin Allam

Date: 27/11/2021
Duration: 1 hour
Total Marks: 20 marks

تعليمات هامة:

- حيلة التليفون المحمول مفتوحا داخل لجنة الامتحان يعتبر حالة غش تستوجب العقاب وإذا كان ضروري الدخول بالمحمول فيوضع مغلقة في الحقيبة.
- لا يسمح بدخول سماعة الأذن أو البلوتوث.
- لا يسمح بدخول أي كتب أو ملزم أو أوراق داخل اللجنة والمخالفة تعتبر حالة غش.

- Exam consists of 20 multiple-choice questions in 3 pages. Each question weights 1 mark.
- Record in the bubble sheet exactly ONE answer for each question.

Qa ⇒ Given the characteristic table of the JK flip-flop:

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

For questions 1 to 4, consider an electronic circuit which consists of the following items:

- A positive edge-triggered JK flip-flop with inputs: clock, J_0 , K_0 , and output: A_0 .
- Another positive edge-triggered JK flip-flop with inputs: clock, J_1 , K_1 , and output: A_1 .
- Logic 1 is connected to both J_0 and K_0 .
- A_0 is connected to both J_1 and K_1 .

1 Assuming $A_1 = 0$ and $A_0 = 0$ while clock input is logic 0. After the clock input becomes logic 1, the values of A_1 and A_0 become:

- ☐ A $A_1 = 0, A_0 = 0$ ☒ B $A_1 = 0, A_0 = 1$ ☐ C $A_1 = 1, A_0 = 0$ ☐ D $A_1 = 1, A_0 = 1$ ☐ E unknown

2 Assuming $A_1 = 0$ and $A_0 = 1$ while clock input is logic 0. After the clock input becomes logic 1, the values of A_1 and A_0 become:

- ☐ A $A_1 = 0, A_0 = 0$ ☐ B $A_1 = 0, A_0 = 1$ ☒ C $A_1 = 1, A_0 = 0$ ☐ D $A_1 = 1, A_0 = 1$ ☐ E unknown

3 Assuming $A_1 = 1$ and $A_0 = 1$ while clock input is logic 0. After the clock input becomes logic 1, the values of A_1 and A_0 become:

- ☒ A $A_1 = 0, A_0 = 0$ ☐ B $A_1 = 0, A_0 = 1$ ☐ C $A_1 = 1, A_0 = 0$ ☐ D $A_1 = 1, A_0 = 1$ ☐ E unknown

4 The above circuit is:

- ☐ A half adder ☒ B shift register ☒ C binary counter ☐ D bus ☐ E other

Qb

\Rightarrow A 4×1 multiplexer with selection inputs S_1 and S_0 selects input 0 when $S_1 S_0 = 00$, selects input 1 when $S_1 S_0 = 01$, selects input 2 when $S_1 S_0 = 10$, and selects input 3 when $S_1 S_0 = 11$.

For questions 5 to 10, consider an electronic circuit which has:

- Inputs: S_1, S_0, C_0 , the binary number $F = F_1 F_0$, and the binary number $G = G_1 G_0$.
- output: the binary number $V = V_1 V_0$.

The circuit consists of the following items:

- A 4×1 multiplexer with selection inputs S_1, S_0 , and 4 inputs: Q_0, Q_1, Q_2, Q_3 , and output: M_0 .
- Another 4×1 multiplexer with selection inputs S_1, S_0 , and 4 inputs: R_0, R_1, R_2, R_3 , and output: M_1 .
- A full-adder with inputs: F_0, M_0, C_0 and outputs: C_1 (carry), V_0 (sum).
- Another full-adder with inputs: F_1, M_1, C_1 and outputs: C_2 (carry), V_1 (sum).
- $\overline{G_0}$ is connected to Q_0 . • $\overline{G_1}$ is connected to R_0 . • G_0 is connected to Q_1 . • G_1 is connected to R_1 .
- Logic 1 is connected to both Q_2 and R_2 . • Logic 0 is connected to both Q_3 and R_3 .

5 After $S_1 = 0, S_0 = 0, C_0 = 0$, the output V will equal to:

- ☐ A $F + G$ ☐ B $F - G$ ☐ C $F + G + 1$ ☒ D $F - G - 1$ ☐ E $F - G + 1$

6 After $S_1 = 0, S_0 = 0, C_0 = 1$, the output V will equal to:

- ☐ A $F + G$ ☒ B $F - G$ ☐ C $F + G + 1$ ☐ D $F - G - 1$ ☐ E $F - G + 1$

7 After $S_1 = 0, S_0 = 1, C_0 = 1$, the output V will equal to:

- ☐ A $F + G$ ☐ B $F - G$ ☒ C $F + G + 1$ ☐ D $F - G - 1$ ☐ E $F - G + 1$

8 After $S_1 = 1, S_0 = 0, C_0 = 0$, the output V will equal to:

- ☐ A $F + G$ ☐ B $F - G$ ☐ C $F + 1$ ☒ D $F - 1$ ☐ E F

9 After $S_1 = 1, S_0 = 0, C_0 = 1$, the output V will equal to:

- ☐ A $F + G$ ☐ B $F - G$ ☐ C $F + 1$ ☐ D $F - 1$ ☒ E F

10 After $S_1 = 1, S_0 = 1, C_0 = 1$, the output V will equal to:

- ☐ A $F + G$ ☐ B $F - G$ ☒ C $F + 1$ ☐ D $F - 1$ ☐ E F

Qc 11 The outputs of 16 registers are connected to the inputs of a bus. Each register stores 32 bits. The bus selects the outputs of one of the input registers according to the selection inputs of the bus. The bus must have the following number of selection inputs:

- ☐ A 3 ☒ B 4 ☐ C 5 ☐ D 16 ☐ E 32

12 The outputs of 16 registers are connected to the inputs of a bus. Each register stores 32 bits. The bus selects the outputs of one of the input registers according to the selection inputs of the bus. The bus must have the following number of multiplexers:

- ☐ A 3 ☐ B 4 ☐ C 5 ☒ D 16 ☐ E 32

13 A memory unit contains 2048 words. Each word is 32 bits. The number of input address lines to this memory unit is:

- ☐ A 5 ☐ B 10 ☒ C 11 ☐ D 16 ☐ E 32

14 A memory unit contains 2048 words. Each word is 32 bits. The number of data output lines out of this memory unit is:

- ☐ A 5 ☐ B 10 ☐ C 11 ☐ D 16 ☒ E 32

15 After applying arithmetic shift right to a 6-bit register containing the binary number 101100 it becomes:

- ☐ A 010110 ☒ B 110110 ☐ C 011001 ☐ D 011000 ☐ E 111100

16 Comparing two numbers to know whether they are equal or not equal, can be done by:

- ☐ A bitwise and ☐ B bitwise or ☒ C bitwise xor ☐ D bitwise complement ☐ E arithmetic shift

17 Consider the ADD instruction which increases the value of the accumulator register by the value located at the effective address. If the instruction uses direct addressing and it contains the address 10 in its address field. The memory word at address 10 contains the value 30, and the memory word at address 30 contains the value 45. After the instruction is executed, the accumulator register increases by:

- ☐ A 10 ☒ B 30 ☐ C 40 ☐ D 45 ☐ E 75

18 Consider the ADD instruction which increases the value of the accumulator register by the value located at the effective address. If the instruction uses indirect addressing and it contains the address 10 in its address field. The memory word at address 10 contains the value 30, and the memory word at address 30 contains the value 45. After the instruction is executed, the accumulator register increases by:

- ☐ A 10 ☐ B 30 ☐ C 40 ☒ D 45 ☐ E 75

19 The following register contains the address of the instruction that is going to be executed:

- ☒ A Program counter ☐ B Accumulator ☐ C Instruction register ☐ D Input register ☐ E Data register

20 Assume that 2 clock cycles are required on average to execute any instruction. The time required to execute a program containing 10,000 instructions on a computer with a clock rate of 5,000,000 clock cycles per second is:

- ☐ A 0.001 seconds ☐ B 0.002 seconds ☒ C 0.004 seconds ☐ D 500 seconds ☐ E 1000 seconds